



## **Звіт**

З лабораторної роботи № 3

З дисципліни “Моделювання комп’ютерних систем”

На тему: “Поведінковий опис цифрового автомата. Перевірка роботи автомата  
за допомогою стенда”


**Варіант – 20**

Виконав: ст.гр. КІ-202  
Побережник Ю.В.  
Перевірив:  
Козак Н.Б.

**Львів 2023**

**Мета роботи :** На базі стенда Elbert V2 – Spartan 3A FPGA, реалізувати цифровий автомат для обчислення значення виразу дотримуючись наступних вимог:

1. Функціонал пристрою повинен бути реалізований згідно отриманого варіанту завдання. Дивись розділ ЗАВДАННЯ:.
2. Пристрій повинен бути ітераційним (АЛП (ALU) повинен виконувати за один такт одну операцію), та реалізованим згідно наступної структурної схеми (Малюнок 1):

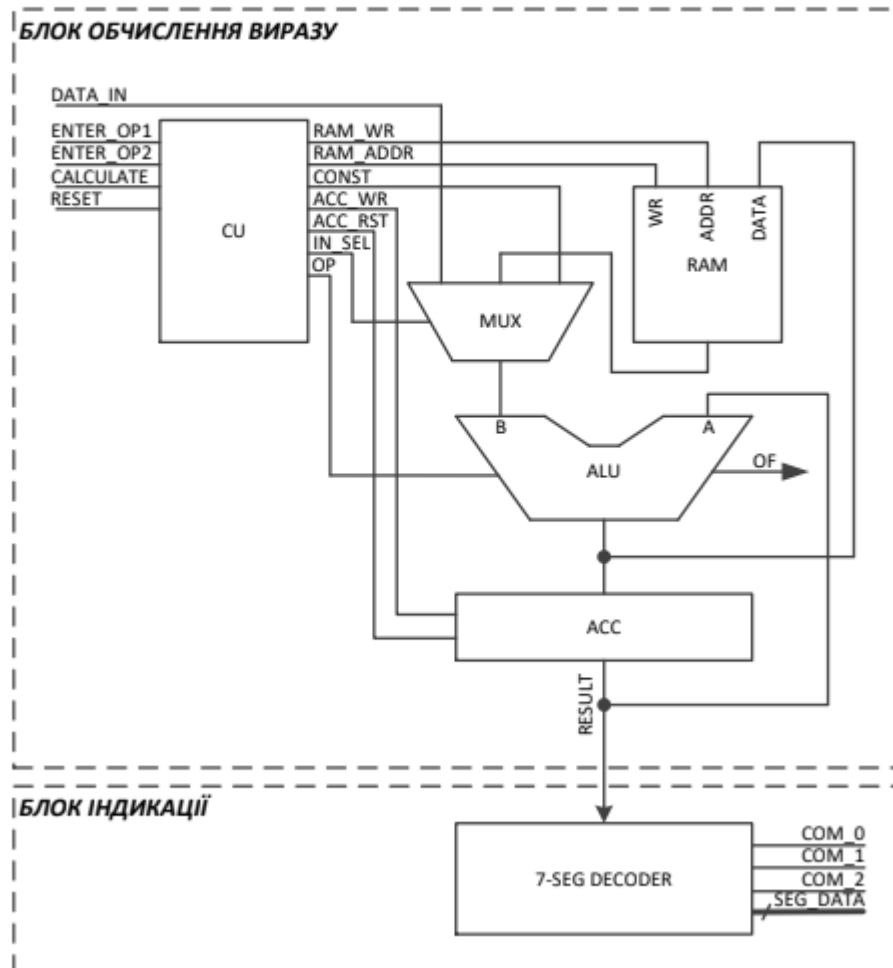

Малюнок 1 - Структурна схема автомата.

## Завдання

6	$((OP1 + OP2) - 2) \ll OP2$
---	-----------------------------

## Виконання роботи:

### Файл CU.vhd:

```
-- Company:
-- Engineer:
--
-- Create Date: 16:27:31 04/27/2023
-- Design Name:
-- Module Name: CU - Behavioral
-- Project Name:
-- Target Devices:
-- Tool versions:
-- Description:
--
-- Dependencies:
--
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
--
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
use IEEE.NUMERIC_STD.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

entity CU_intf is
    port(CLOCK : IN STD_LOGIC;
         RESET : IN STD_LOGIC;
         ENTER_OP1 : IN STD_LOGIC;
         ENTER_OP2 : IN STD_LOGIC;
         CALCULATE : IN STD_LOGIC;

         RAM_WR : OUT STD_LOGIC;
         RAM_ADDR_BUS : OUT STD_LOGIC_VECTOR(1 downto 0);
```

```

        CONSTANT_BUS      : OUT STD_LOGIC_VECTOR(7 downto 0):=
"00000010";
        ACC_WR : OUT STD_LOGIC;
        ACC_RST : OUT STD_LOGIC;
        IN_SEL : OUT STD_LOGIC_VECTOR(1 downto 0);
        OP_CODE_BUS : OUT STD_LOGIC_VECTOR(1 downto 0)
    );
end CU_intf;

```

architecture CU\_arch of CU\_intf is

```

type cu_state_type is (cu_rst, cu_idle, cu_load_op1, cu_load_op2, cu_run_calc0,
cu_run_calc1, cu_run_calc2, cu_run_calc3, cu_finish);
signal cu_cur_state : cu_state_type;
signal cu_next_state : cu_state_type;

```

```

begin
CONSTANT_BUS      <= "00000010";
CU_SYNC_PROC: process (CLOCK)
begin
    if (rising_edge(CLOCK)) then
        if (RESET = '1') then
            cu_cur_state <= cu_rst;
        else
            cu_cur_state <= cu_next_state;
        end if;
    end if;
end process;

```

```

        CUNEXT_STATE_DECODE: process (cu_cur_state, ENTER_OP1,
ENTER_OP2, CALCULATE)

```

```

begin
    --declare default state for next_state to avoid latches
    cu_next_state <= cu_cur_state; --default is to stay in current state
    --insert statements to decode next_state
    --below is a simple example
    case(cu_cur_state) is
        when cu_rst =>
            cu_next_state <= cu_idle;
        when cu_idle =>
            if (ENTER_OP1 = '1') then
                cu_next_state <= cu_load_op1;
            elsif (ENTER_OP2 = '1') then
                cu_next_state <= cu_load_op2;
            elsif (CALCULATE = '1') then
                cu_next_state <= cu_run_calc0;
            else

```

```

        cu_next_state <= cu_idle;
    end if;
    when cu_load_op1 =>
        cu_next_state <= cu_idle;
    when cu_load_op2 =>
        cu_next_state <= cu_idle;
    when cu_run_calc0 =>
        cu_next_state <= cu_run_calc1;
    when cu_run_calc1 =>
        cu_next_state <= cu_run_calc2;
    when cu_run_calc2 =>
        cu_next_state <= cu_run_calc3;
    when cu_run_calc3 =>
        cu_next_state <= cu_finish;
    when cu_finish =>
        cu_next_state <= cu_finish;
    when others =>
        cu_next_state <= cu_idle;
    end case;
end process;

```

CU\_OUTPUT\_DECODE: process (cu\_cur\_state)  
begin

```

    case(cu_cur_state) is
        when cu_rst =>
            IN_SEL <= "00";
            OP_CODE_BUS <= "00";
            RAM_ADDR_BUS <= "00";
            RAM_WR <= '0';
            ACC_RST <= '1';
            ACC_WR <= '0';
        when cu_idle =>
            IN_SEL <= "00";
            OP_CODE_BUS <= "00";
            RAM_ADDR_BUS <= "00";
            RAM_WR <= '0';
            ACC_RST <= '0';
            ACC_WR <= '0';
        when cu_load_op1 =>
            IN_SEL <= "00";
            OP_CODE_BUS <= "00";
            RAM_ADDR_BUS <= "00";
            RAM_WR <= '1';
            ACC_RST <= '0';
            ACC_WR <= '1';
        when cu_load_op2 =>

```

```

        IN_SEL                <= "00";
        OP_CODE_BUS <= "00";
        RAM_ADDR_BUS <= "01";
        RAM_WR          <= '1';
        ACC_RST         <= '0';
        ACC_WR          <= '1';
    when cu_run_calc0 =>
        IN_SEL                <= "01";
        OP_CODE_BUS <= "00";
        RAM_ADDR_BUS <= "00";
        RAM_WR          <= '0';
        ACC_RST         <= '0';
        ACC_WR          <= '1';
    when cu_run_calc1 =>
        IN_SEL                <= "01";
        OP_CODE_BUS <= "01";
        RAM_ADDR_BUS <= "01";
        RAM_WR          <= '0';
        ACC_RST         <= '0';
        ACC_WR          <= '1';
    when cu_run_calc2 =>
        IN_SEL                <= "10";
        OP_CODE_BUS <= "10";
        RAM_ADDR_BUS <= "01";
        RAM_WR          <= '0';
        ACC_RST         <= '0';
        ACC_WR          <= '1';
    when cu_run_calc3 =>
        IN_SEL                <= "01";
        OP_CODE_BUS <= "11";
        RAM_ADDR_BUS <= "01";
        RAM_WR          <= '0';
        ACC_RST         <= '0';
        ACC_WR          <= '1';
    when cu_finish    =>
        IN_SEL                <= "00";
        OP_CODE_BUS <= "00";
        RAM_ADDR_BUS <= "00";
        RAM_WR          <= '0';
        ACC_RST         <= '0';
        ACC_WR          <= '0';
    when others        =>
        IN_SEL                <= "00";
        OP_CODE_BUS <= "00";
        RAM_ADDR_BUS <= "00";
        RAM_WR          <= '0';
        ACC_RST         <= '0';

```


```

        ACC_WR                                     <= '0';
    end case;
end process;
end CU_arch;

```

**Элемент CU:**

## CU\_intf

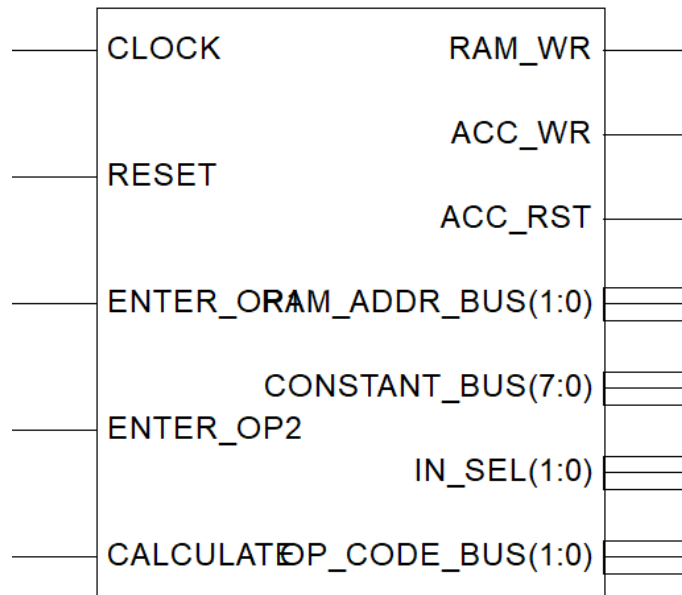

**Файл MUX.vhd:**

```

-----
-- Company:
-- Engineer:
--
-- Create Date: 15:06:55 04/27/2023
-- Design Name:
-- Module Name: MUX - Behavioral
-- Project Name:
-- Target Devices:
-- Tool versions:
-- Description:
--
-- Dependencies:
--
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
--
-----

```

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

```

```

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values

```

```

use IEEE.NUMERIC_STD.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM.VComponents.all;


entity MUX_intf is
    port(
        DATA_IN          : IN STD_LOGIC_VECTOR(7 downto 0);
        CONSTANT_BUS : IN STD_LOGIC_VECTOR(7 downto 0);
        RAM_DATA_OUT_BUS: IN STD_LOGIC_VECTOR(7 downto 0);
        IN_SEL              : IN STD_LOGIC_VECTOR(1 downto
0);
        IN_SEL_OUT_BUS : OUT std_logic_vector(7 downto 0)
    );
end MUX_intf;

architecture MUX_arch of MUX_intf is

begin
INSEL_A_MUX : process(DATA_IN, CONSTANT_BUS,
RAM_DATA_OUT_BUS, IN_SEL)
    begin
        if(IN_SEL = "00") then
            IN_SEL_OUT_BUS <= DATA_IN;
        elsif(IN_SEL = "01") then
            IN_SEL_OUT_BUS <= RAM_DATA_OUT_BUS;
        else
            IN_SEL_OUT_BUS <= CONSTANT_BUS;
        end if;
    end process INSEL_A_MUX;
end MUX_arch;
Элемент MUX:

```



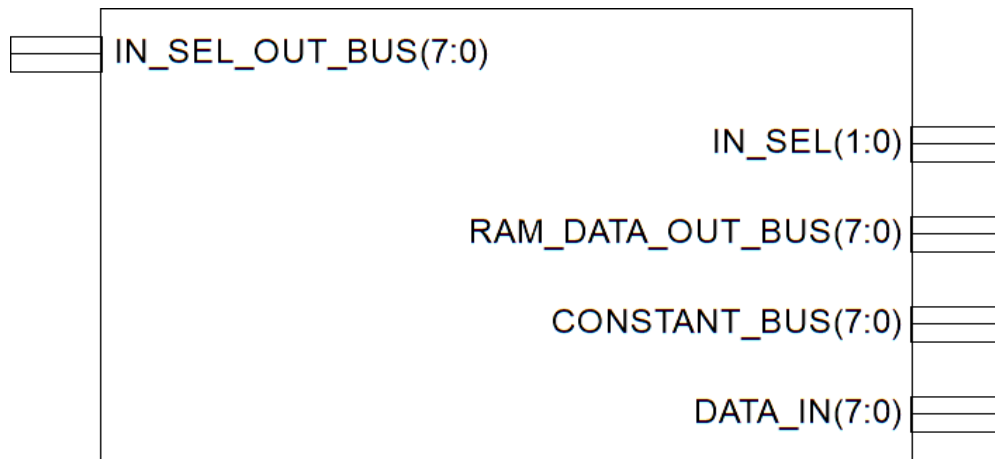

## MUX\_intf

### Файл RAM.vhd:

```

-----
-- Company:
-- Engineer:
--
-- Create Date: 16:49:14 04/27/2023
-- Design Name:
-- Module Name: RAM - Behavioral
-- Project Name:
-- Target Devices:
-- Tool versions:
-- Description:
--
-- Dependencies:
--
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
--
-----

```

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

```

```

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
use IEEE.NUMERIC_STD.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

```

```

-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

```

```

entity RAM_intf is
port(
    RAM_WR          : IN STD_LOGIC;
    RAM_ADDR_BUS    : IN STD_LOGIC_VECTOR(1 downto
0);
    ACC_DATA_IN_BUS : IN STD_LOGIC_VECTOR(7 downto 0);
    RAM_DATA_OUT_BUS: OUT STD_LOGIC_VECTOR(7 downto 0);
    CLOCK           : IN STD_LOGIC
    );
end RAM_intf;

```

```

architecture RAM_arch of RAM_intf is
type ram_type is array (3 downto 0) of STD_LOGIC_VECTOR(7 downto 0);
signal RAM_UNIT          : ram_type;
signal RAM_DATA_IN_BUS : STD_LOGIC_VECTOR(7 downto 0);

```

```

begin
    RAM_DATA_IN_BUS <= ACC_DATA_IN_BUS;

    RAM : process(CLOCK, RAM_ADDR_BUS, RAM_UNIT)
    begin
        if (rising_edge(CLOCK)) then
            if (RAM_WR = '1') then
                RAM_UNIT(conv_integer(RAM_ADDR_BUS)) <=
RAM_DATA_IN_BUS;
            end if;
        end if;
        RAM_DATA_OUT_BUS <=
RAM_UNIT(conv_integer(RAM_ADDR_BUS));
    end process RAM;

```


```

end RAM_arch;

```

**Элемент RAM:**

# RAM\_intf

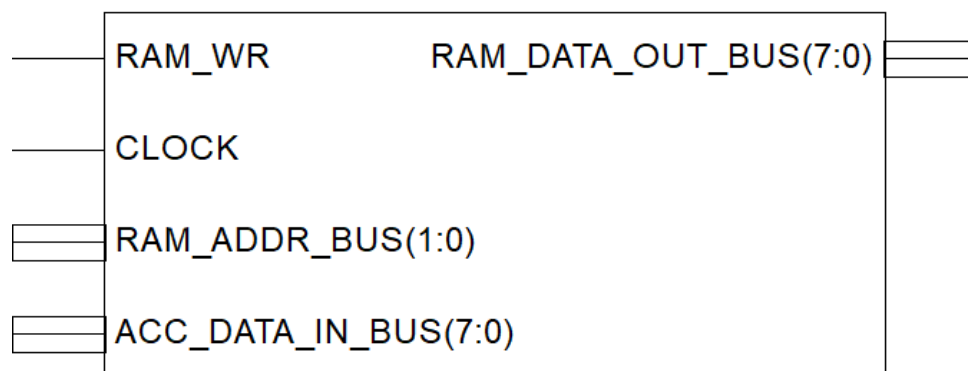

## Файл ALU.vhd:

```
-----
-- Company:
-- Engineer:
--
-- Create Date: 16:13:46 04/27/2023
-- Design Name:
-- Module Name: ALU - Behavioral
-- Project Name:
-- Target Devices:
-- Tool versions:
-- Description:
--
-- Dependencies:
--
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
--
-----

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
use IEEE.NUMERIC_STD.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

entity ALU_intf is
port(
    IN_SEL_OUT_BUS : IN STD_LOGIC_VECTOR(7 downto 0);
    ACC_DATA_OUT_BUS : IN STD_LOGIC_VECTOR(7 downto 0);
    OP_CODE_BUS : IN STD_LOGIC_VECTOR(1 downto 0);
    ACC_DATA_IN_BUS : OUT STD_LOGIC_VECTOR(7 downto 0);
    OVER_FLOW : OUT STD_LOGIC
    --OF - overflow
);
end ALU_intf;

architecture ALU_arch of ALU_intf is
begin
```

```

ALU : process(OP_CODE_BUS, IN_SEL_OUT_BUS, ACC_DATA_OUT_BUS)
    variable A : unsigned(7 downto 0);
    variable B : unsigned(7 downto 0);
    variable temp : std_logic_vector(8 downto 0);
begin
    A := unsigned(ACC_DATA_OUT_BUS);
    B := unsigned(IN_SEL_OUT_BUS);

    if OP_CODE_BUS = "00" then
        ACC_DATA_IN_BUS <= STD_LOGIC_VECTOR(B);
    elsif OP_CODE_BUS = "01" then
        temp := STD_LOGIC_VECTOR('0' & A) +
STD_LOGIC_VECTOR('0' & B);
        if (temp(8) = '1') then
            OVER_FLOW <= '1';
        else
            OVER_FLOW <= '0';
        end if;
        ACC_DATA_IN_BUS <= temp(7 downto 0);
    elsif OP_CODE_BUS = "10" then
        temp := STD_LOGIC_VECTOR('0' & A) - STD_LOGIC_VECTOR('0'
& B);
        if (temp(8) = '1') then
            OVER_FLOW <= '1';
        else
            OVER_FLOW <= '0';
        end if;
        ACC_DATA_IN_BUS <= temp(7 downto 0);
    elsif OP_CODE_BUS = "11" then
        case(B) is --case(B) is
            when x"00"      => ACC_DATA_IN_BUS <=
STD_LOGIC_VECTOR(A sll 0);
            when x"01"      => ACC_DATA_IN_BUS <=
STD_LOGIC_VECTOR(A sll 1);
            when x"02"      => ACC_DATA_IN_BUS <=
STD_LOGIC_VECTOR(A sll 2);
            when x"03"      => ACC_DATA_IN_BUS <=
STD_LOGIC_VECTOR(A sll 3);
            when x"04"      => ACC_DATA_IN_BUS <=
STD_LOGIC_VECTOR(A sll 4);
            when x"05"      => ACC_DATA_IN_BUS <=
STD_LOGIC_VECTOR(A sll 5);
            when x"06"      => ACC_DATA_IN_BUS <=
STD_LOGIC_VECTOR(A sll 6);
            when x"07"      => ACC_DATA_IN_BUS <=
STD_LOGIC_VECTOR(A sll 7);

```

```


                                when others => ACC_DATA_IN_BUS <=
STD_LOGIC_VECTOR(A sll 0);
                                end case;
                                else
                                ACC_DATA_IN_BUS <= "00000000";
                                end if;
                                end process ALU;

                                end ALU_arch;

```

## Элемент ALU:

# ALU\_intf

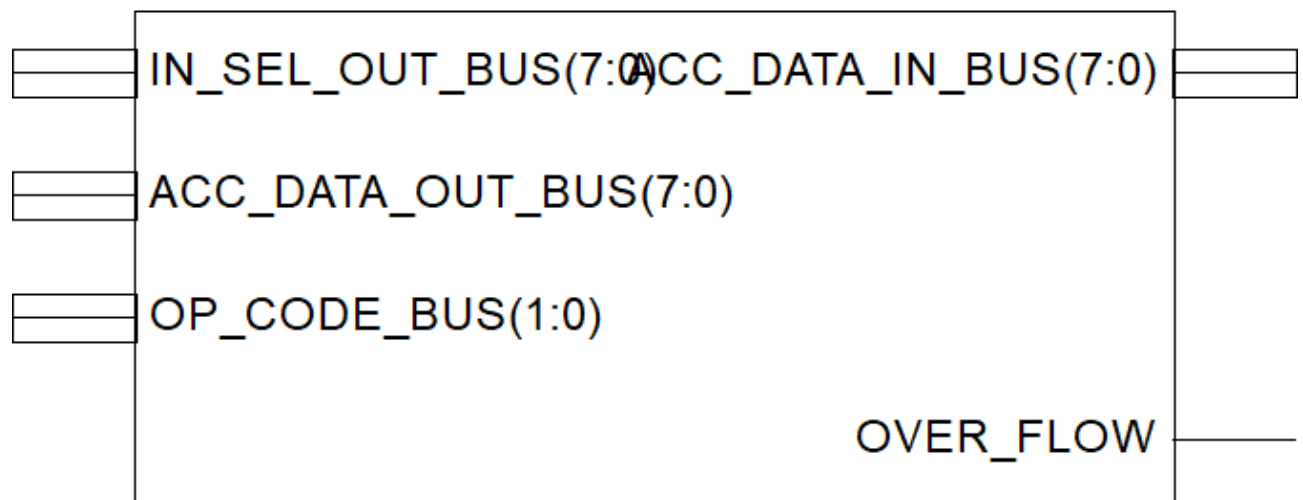

## Файл ACC.vhd:

```

-----
-- Company:
-- Engineer:
--
-- Create Date: 15:27:57 04/27/2023
-- Design Name:
-- Module Name: ACC - Behavioral
-- Project Name:
-- Target Devices:
-- Tool versions:
-- Description:
--
-- Dependencies:
--
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
--
-----

```

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
use IEEE.NUMERIC_STD.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

entity ACC_intf is
port(
    CLOCK          : IN STD_LOGIC;
    ACC_RST        : IN STD_LOGIC;
    ACC_WR         : IN STD_LOGIC;
    ACC_DATA_IN_BUS : IN STD_LOGIC_VECTOR(7 downto 0);
    ACC_DATA_OUT_BUS : OUT STD_LOGIC_VECTOR(7 downto 0)
);
end ACC_intf;


architecture ACC_arch of ACC_intf is

    signal ACC_DATA          : STD_LOGIC_VECTOR(7 downto 0);

begin
    ACC : process(CLOCK, ACC_DATA)
    begin
        if (rising_edge(CLOCK)) then
            if(ACC_RST = '1') then
                ACC_DATA <= "00000000";
            elsif (ACC_WR = '1') then
                ACC_DATA <= ACC_DATA_IN_BUS;
            end if;
        end if;
        ACC_DATA_OUT_BUS <= ACC_DATA;
    end process ACC;
end ACC_arch;
Элемент ACC:

```

# ACC\_intf

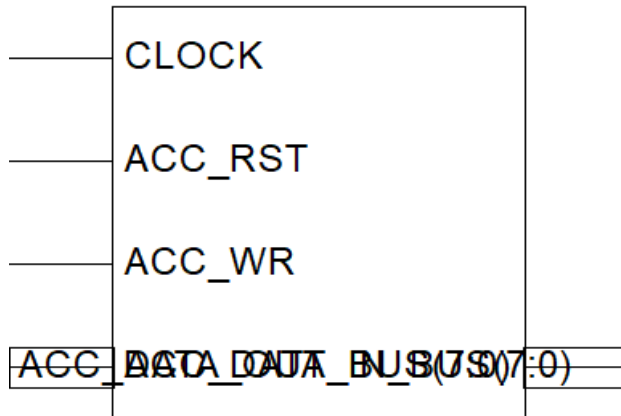

**Файл SEGDEC.vhd:**

```

-----
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
use IEEE.NUMERIC_STD.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

entity SEGDEC_intf is
port(
    CLOCK          : IN STD_LOGIC;
    ACC_DATA_OUT_BUS : IN STD_LOGIC_VECTOR(7 downto 0);
    RESET          : IN STD_LOGIC;
    OverFlow_IN    : IN STD_LOGIC;
    COMM_ONES      : OUT STD_LOGIC;
    COMM_DECS      : OUT STD_LOGIC;
    COMM_HUNDREDS  : OUT STD_LOGIC;
    SEG_A          : OUT STD_LOGIC;
    SEG_B          : OUT STD_LOGIC;
    SEG_C          : OUT STD_LOGIC;
    SEG_D          : OUT STD_LOGIC;
    SEG_E          : OUT STD_LOGIC;
    SEG_F          : OUT STD_LOGIC;
    SEG_G          : OUT STD_LOGIC;
    DP             : OUT STD_LOGIC;
    OverFlow_OUT   : OUT STD_LOGIC := '0'

```

```

    );
end SEGDEC_intf;

```

```

architecture SEGDEC_arch of SEGDEC_intf is
signal ONES_BUS : STD_LOGIC_VECTOR(3 downto 0) := "0000";
signal DECS_BUS : STD_LOGIC_VECTOR(3 downto 0) := "0000";
signal HONDREDS_BUS : STD_LOGIC_VECTOR(3 downto 0) := "0000";
begin

```

```

OVERFLOW_INDICATE : process(OverFlow_IN, RESET)
begin
    --if rising_edge(CLOCK) then
    if (RESET = '1') then
        OverFlow_OUT <= '0';
    elsif (RESET = '0' and OverFlow_IN = '1') then
        OverFlow_OUT <= '1';
    end if;
    --end if;
end process OVERFLOW_INDICATE;

```

```

BIN_TO_BCD : process (ACC_DATA_OUT_BUS)
variable hex_src : STD_LOGIC_VECTOR(7 downto 0) ;
variable bcd : STD_LOGIC_VECTOR(11 downto 0) ;
begin
    bcd := (others => '0') ;
    hex_src := ACC_DATA_OUT_BUS;

    for i in hex_src'range loop
        if bcd(3 downto 0) > "0100" then
            bcd(3 downto 0) := bcd(3 downto 0) + "0011" ;
        end if ;
        if bcd(7 downto 4) > "0100" then
            bcd(7 downto 4) := bcd(7 downto 4) + "0011" ;
        end if ;
        if bcd(11 downto 8) > "0100" then
            bcd(11 downto 8) := bcd(11 downto 8) + "0011" ;
        end if ;

        bcd := bcd(10 downto 0) & hex_src(hex_src'left) ; -- shift bcd + 1 new entry
        hex_src := hex_src(hex_src'left - 1 downto hex_src'right) & '0' ; -- shift src +
pad with 0
    end loop ;

    HONDREDS_BUS <= bcd (11 downto 8);
    DECS_BUS <= bcd (7 downto 4);
    ONES_BUS <= bcd (3 downto 0);

```



```

end process BIN_TO_BCD;

INDICATE : process(CLOCK)
    type DIGIT_TYPE is (ONES, DECS, HUNDREDS);

    variable CUR_DIGIT    : DIGIT_TYPE := ONES;
    variable DIGIT_VAL    : STD_LOGIC_VECTOR(3 downto 0) :=
"0000";
    variable DIGIT_CTRL   : STD_LOGIC_VECTOR(6 downto 0) :=
"0000000";
    variable COMMONS_CTRL : STD_LOGIC_VECTOR(2 downto 0) :=
"000";

    begin
        if (rising_edge(CLOCK)) then
            if(RESET = '0') then
                case CUR_DIGIT is
                    when ONES =>
                        DIGIT_VAL := ONES_BUS;
                        CUR_DIGIT := DECS;
                        COMMONS_CTRL := "001";
                    when DECS =>
                        DIGIT_VAL := DECS_BUS;
                        CUR_DIGIT := HUNDREDS;
                        COMMONS_CTRL := "010";
                    when HUNDREDS =>
                        DIGIT_VAL := HONDREDS_BUS;
                        CUR_DIGIT := ONES;
                        COMMONS_CTRL := "100";
                    when others =>
                        DIGIT_VAL := ONES_BUS;
                        CUR_DIGIT := ONES;
                        COMMONS_CTRL := "000";
                end case;

                case DIGIT_VAL is
                    --abcdefg
                    when "0000" => DIGIT_CTRL := "1111110";
                    when "0001" => DIGIT_CTRL := "0110000";
                    when "0010" => DIGIT_CTRL := "1101101";
                    when "0011" => DIGIT_CTRL := "1111001";
                    when "0100" => DIGIT_CTRL := "0110011";
                    when "0101" => DIGIT_CTRL := "1011011";
                    when "0110" => DIGIT_CTRL := "1011111";
                    when "0111" => DIGIT_CTRL := "1110000";
                    when "1000" => DIGIT_CTRL := "1111111";
                    when "1001" => DIGIT_CTRL := "1111011";
                end case;
            end if;
        end if;
    end process;

```

```

        when others => DIGIT_CTRL := "0000000";
    end case;
else
    DIGIT_VAL := ONES_BUS;
    CUR_DIGIT := ONES;
    COMMONS_CTRL := "000";
end if;


COMM_ONES    <= COMMONS_CTRL(0);
COMM_DECS    <= COMMONS_CTRL(1);
COMM_HUNDREDS <= COMMONS_CTRL(2);

SEG_A <= DIGIT_CTRL(6);
SEG_B <= DIGIT_CTRL(5);
SEG_C <= DIGIT_CTRL(4);
SEG_D <= DIGIT_CTRL(3);
SEG_E <= DIGIT_CTRL(2);
SEG_F <= DIGIT_CTRL(1);
SEG_G <= DIGIT_CTRL(0);
DP    <= '0';


    end if;
end process INDICATE;
end SEGDEC_arch;
Элемент SEGDEC:

```

# SEGDEC\_intf

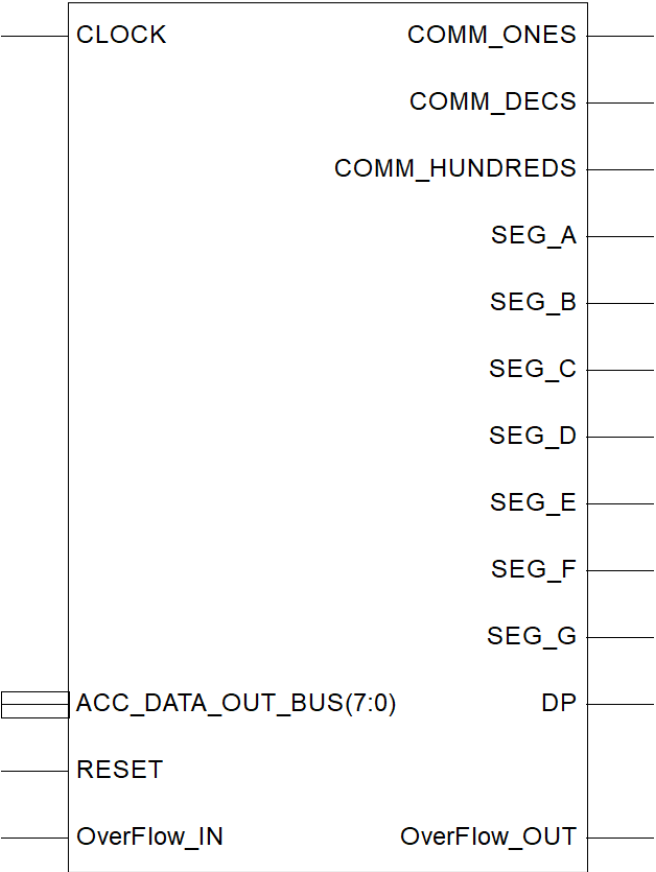

## Схема для Top Level:

 

## Файл Constraints.ucf:

### UCF for ElbertV2 Development Board

CONFIG VCCAUX = "3.3" ;

# Clock 12 MHz

NET "CLOCK" LOC = P129 | IOSTANDARD = LVCMOS33 | PERIOD  
= 12MHz;

#### LED

NET "OVERFLOW" LOC = P46 | IOSTANDARD = LVCMOS33 |  
SLEW = SLOW | DRIVE = 12;

#### Seven Segment Display

NET "A\_OUT" LOC = P117 | IOSTANDARD = LVCMOS33 | SLEW = SLOW  
| DRIVE = 12;

NET "B\_OUT" LOC = P116 | IOSTANDARD = LVCMOS33 | SLEW = SLOW  
| DRIVE = 12;

NET "C\_OUT" LOC = P115 | IOSTANDARD = LVCMOS33 | SLEW = SLOW  
| DRIVE = 12;

NET "D\_OUT" LOC = P113 | IOSTANDARD = LVCMOS33 | SLEW = SLOW  
| DRIVE = 12;

NET "E\_OUT" LOC = P112 | IOSTANDARD = LVCMOS33 | SLEW = SLOW  
| DRIVE = 12;

NET "F\_OUT" LOC = P111 | IOSTANDARD = LVCMOS33 | SLEW = SLOW  
| DRIVE = 12;

NET "G\_OUT" LOC = P110 | IOSTANDARD = LVCMOS33 | SLEW = SLOW  
| DRIVE = 12;

NET "DP\_OUT" LOC = P114 | IOSTANDARD = LVCMOS33 | SLEW =  
SLOW | DRIVE = 12;

NET "COMMON\_2\_OUT" LOC = P124 | IOSTANDARD = LVCMOS33 |  
SLEW = SLOW | DRIVE = 12;

NET "COMMON\_1\_OUT" LOC = P121 | IOSTANDARD = LVCMOS33 |  
SLEW = SLOW | DRIVE = 12;

NET "COMMON\_0\_OUT" LOC = P120 | IOSTANDARD = LVCMOS33 |  
SLEW = SLOW | DRIVE = 12;

#### DP Switches

NET "DATA\_IN(0)" LOC = P70 | PULLUP | IOSTANDARD =  
LVCMOS33 | SLEW = SLOW | DRIVE = 12;

```

NET "DATA_IN(1)"      LOC = P69  | PULLUP | IOSTANDARD =
LVCMOS33 | SLEW = SLOW | DRIVE = 12;
NET "DATA_IN(2)"      LOC = P68  | PULLUP | IOSTANDARD =
LVCMOS33 | SLEW = SLOW | DRIVE = 12;
NET "DATA_IN(3)"      LOC = P64  | PULLUP | IOSTANDARD =
LVCMOS33 | SLEW = SLOW | DRIVE = 12;
NET "DATA_IN(4)"      LOC = P63  | PULLUP | IOSTANDARD =
LVCMOS33 | SLEW = SLOW | DRIVE = 12;
NET "DATA_IN(5)"      LOC = P60  | PULLUP | IOSTANDARD =
LVCMOS33 | SLEW = SLOW | DRIVE = 12;
NET "DATA_IN(6)"      LOC = P59  | PULLUP | IOSTANDARD =
LVCMOS33 | SLEW = SLOW | DRIVE = 12;
NET "DATA_IN(7)"      LOC = P58  | PULLUP | IOSTANDARD =
LVCMOS33 | SLEW = SLOW | DRIVE = 12;

```

### Switches

```

NET "ENTER_OP1"      LOC = P80  | PULLUP | IOSTANDARD =
LVCMOS33 | SLEW = SLOW | DRIVE = 12;
NET "ENTER_OP2"      LOC = P79  | PULLUP | IOSTANDARD =
LVCMOS33 | SLEW = SLOW | DRIVE = 12;
NET "CALCULATE"      LOC = P78  | PULLUP | IOSTANDARD =
LVCMOS33 | SLEW = SLOW | DRIVE = 12;
NET "RESET"          LOC = P75  | PULLUP | IOSTANDARD = LVCMOS33 |
SLEW = SLOW | DRIVE = 12;

```

### Файл TestTopLevel.vhd:

```

-- Vhdl test bench created from schematic D:\Lab_3_Example\TopLevel.sch - Mon
May 01 21:40:52 2023

```

```
--
```

```
-- Notes:
```

```

-- 1) This testbench template has been automatically generated using types
-- std_logic and std_logic_vector for the ports of the unit under test.
-- Xilinx recommends that these types always be used for the top-level
-- I/O of a design in order to guarantee that the testbench will bind
-- correctly to the timing (post-route) simulation model.
-- 2) To use this template as your testbench, change the filename to any
-- name of your choice with the extension .vhd, and use the "Source->Add"
-- menu in Project Navigator to import the testbench. Then
-- edit the user defined section below, adding code to generate the
-- stimulus for your design.

```

```
--
```

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.ALL;

```

```

LIBRARY UNISIM;
USE UNISIM.Vcomponents.ALL;
ENTITY TopLevel_TopLevel_sch_tb IS
END TopLevel_TopLevel_sch_tb;
ARCHITECTURE behavioral OF TopLevel_TopLevel_sch_tb IS

```

```

    COMPONENT TopLevel
    PORT( RESE      :    IN   STD_LOGIC;
          ENTER_OP1 :    IN   STD_LOGIC;
          ENTER_OP2 :    IN   STD_LOGIC;
          CALCULATE  :    IN   STD_LOGIC;
          COMMON_0_OUT :    OUT STD_LOGIC;
          COMMON_1_OUT :    OUT STD_LOGIC;
          COMMON_2_OUT :    OUT STD_LOGIC;
          A_OUT       :    OUT STD_LOGIC;
          B_OUT       :    OUT STD_LOGIC;
          C_OUT       :    OUT STD_LOGIC;
          D_OUT       :    OUT STD_LOGIC;
          E_OUT       :    OUT STD_LOGIC;
          F_OUT       :    OUT STD_LOGIC;
          G_OUT       :    OUT STD_LOGIC;
          DP_OUT      :    OUT STD_LOGIC;
          CLOCK       :    IN   STD_LOGIC;
          DATA_IN    :    IN   STD_LOGIC_VECTOR (7 DOWNT0 0);
          OVER_FLOW   :    OUT STD_LOGIC);
    END COMPONENT;

```

```

        signal op1 : STD_LOGIC_VECTOR(7 DOWNT0 0);
        signal op2 : STD_LOGIC_VECTOR(7 DOWNT0 0);
    SIGNAL RESE :    STD_LOGIC;
    SIGNAL ENTER_OP1      :    STD_LOGIC;
    SIGNAL ENTER_OP2      :    STD_LOGIC;
    SIGNAL CALCULATE      :    STD_LOGIC;
    SIGNAL COMMON_0_OUT    :    STD_LOGIC;
    SIGNAL COMMON_1_OUT    :    STD_LOGIC;
    SIGNAL COMMON_2_OUT    :    STD_LOGIC;
    SIGNAL A_OUT           :    STD_LOGIC;
    SIGNAL B_OUT           :    STD_LOGIC;
    SIGNAL C_OUT           :    STD_LOGIC;
    SIGNAL D_OUT           :    STD_LOGIC;
    SIGNAL E_OUT           :    STD_LOGIC;
    SIGNAL F_OUT           :    STD_LOGIC;
    SIGNAL G_OUT           :    STD_LOGIC;
    SIGNAL DP_OUT          :    STD_LOGIC;
    SIGNAL CLOCK           :    STD_LOGIC;
    SIGNAL DATA_IN        :    STD_LOGIC_VECTOR (7 DOWNT0 0);
    SIGNAL OVER_FLOW       :    STD_LOGIC;

```

```
constant CLK_period: time := 1 us;  
constant TC_period: time := 65536 us;
```

```
BEGIN
```

```
UUT: TopLevel PORT MAP(  
    RESE => RESE,  
    ENTER_OP1 => ENTER_OP1,  
    ENTER_OP2 => ENTER_OP2,  
    CALCULATE => CALCULATE,  
    COMMON_0_OUT => COMMON_0_OUT,  
    COMMON_1_OUT => COMMON_1_OUT,  
    COMMON_2_OUT => COMMON_2_OUT,  
    A_OUT => A_OUT,  
    B_OUT => B_OUT,  
    C_OUT => C_OUT,  
    D_OUT => D_OUT,  
    E_OUT => E_OUT,  
    F_OUT => F_OUT,  
    G_OUT => G_OUT,  
    DP_OUT => DP_OUT,  
    CLOCK => CLOCK,  
    DATA_IN => DATA_IN,  
    OVER_FLOW => OVER_FLOW  
);
```

```
CLK_process : process  
begin  
    CLOCK <= '1';  
    wait for CLK_period/2;  
    CLOCK <= '0';  
    wait for CLK_period/2;  
end process CLK_process;
```

```
stim_proc: process  
begin  
    RESE <= '1';  
    ENTER_OP1 <= '0';  
    ENTER_OP2 <= '0';  
    CALCULATE <= '0';  
    DATA_IN <=(others => '0');  
  
    wait for 2*CLK_period;  
    RESE <='0';
```

```

wait for 4*TC_period;
ENTER_OP1 <='1';
DATA_IN  <= op1;

wait for 2*TC_period;
ENTER_OP1 <='0';

wait for 4*TC_period;
ENTER_OP2 <='1';
DATA_IN  <= op2;


wait for 2*TC_period;
ENTER_OP2 <='0';
wait for 4*TC_period;

CALCULATE <= '1';
wait for 8*TC_period;
wait;
end process stim_proc; --1.835 s
END;




```


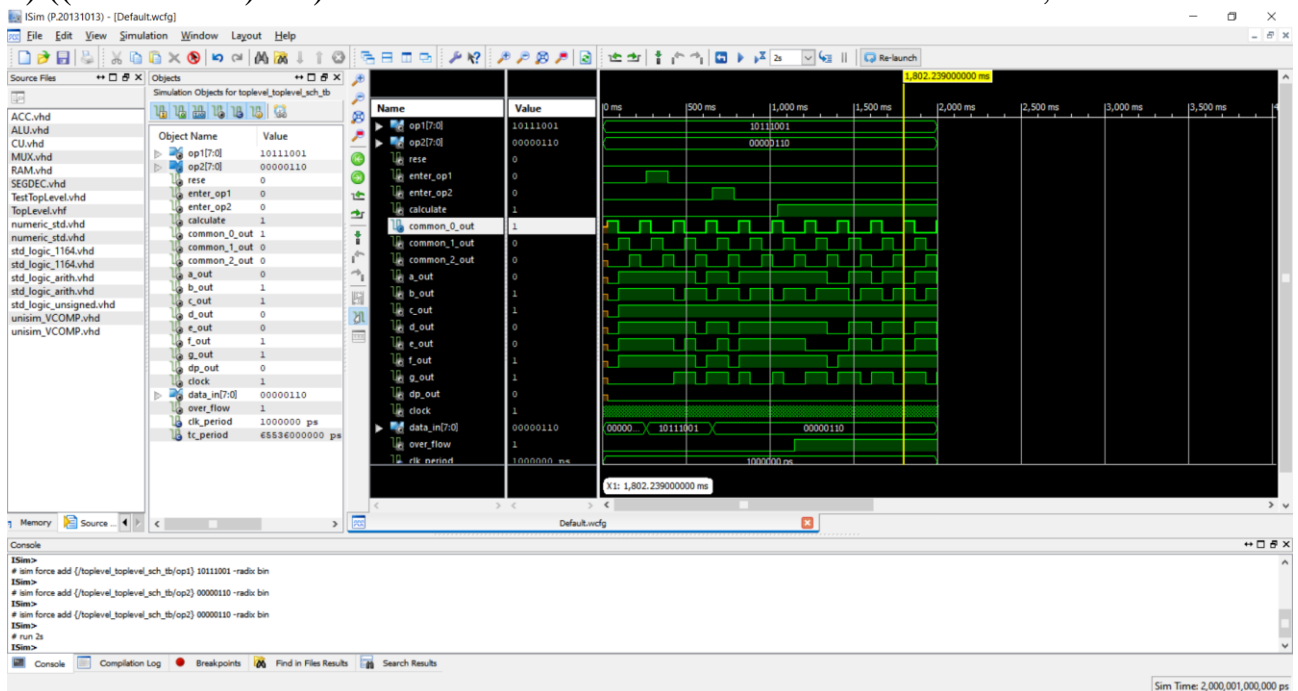
### Перевірка результату

OP1=10111001;  
 OP2=00000110;  
 $((OP1 + OP2) - 2) \ll OP2 = 01000000$ ;  
 1)  $(OP1 + OP2) = 10111001 + 00000110 = 10111111$ ;  
 2)  $(OP1 + OP2) - 2 = 10111111 - 00000010 = 10111101$ ;  
 3)  $((OP1 + OP2) - 2) \ll OP2 = 10111101 \ll 00000110 = 01000000$ ;





 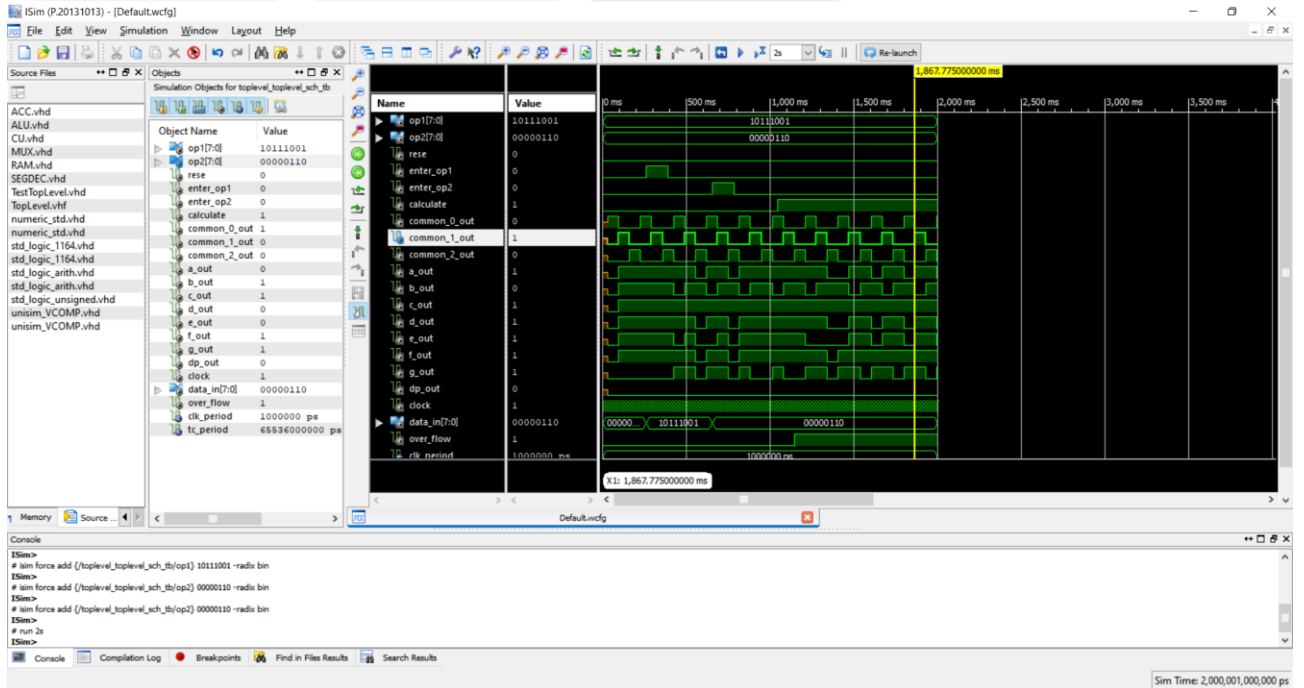 

 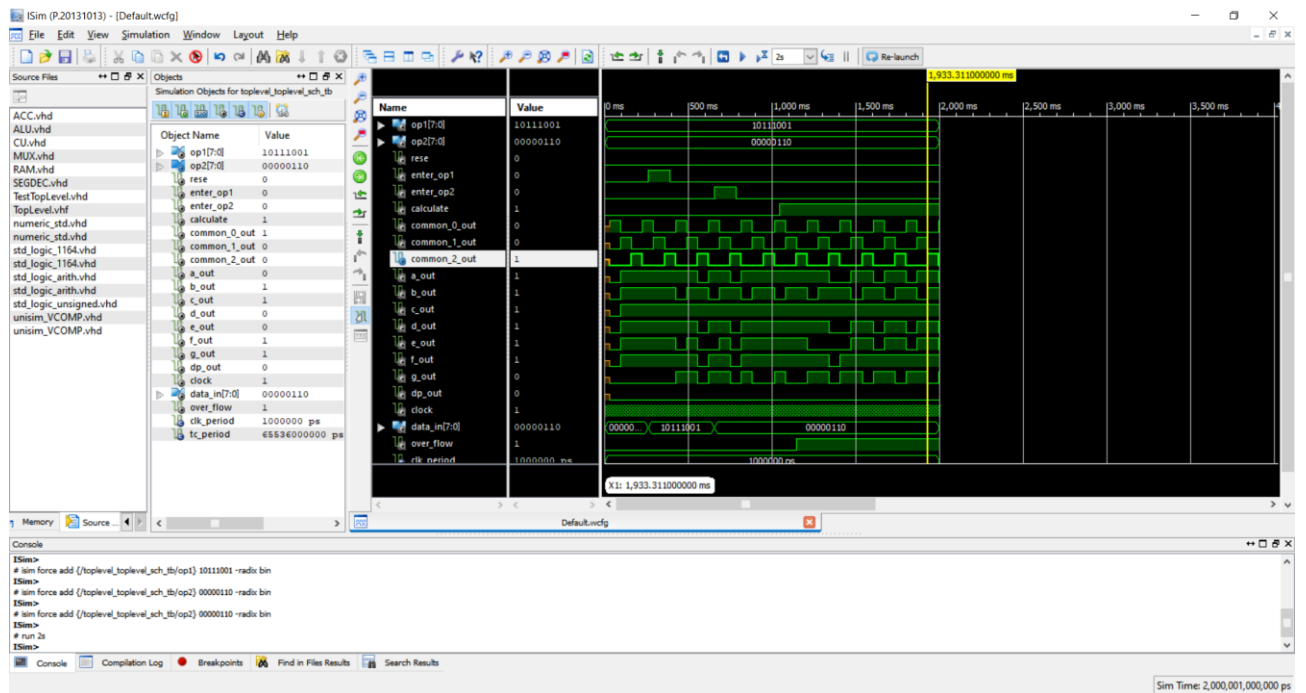

**Висновок:** Під час даної лабораторної роботи, я на базі стенда Elbert V2 – Spartan 3A FPGA, реалізував цифровий автомат для обчислення значення заданого виразу.